

Assignment 1: Programming a Traffic-Light Controller

Overview

In this assignment, you will program a traffic-light controller (Figure 1). Your program will handle multiple tasks, some of which are executed periodically, and others of which are triggered asynchronously. Periodic tasks are those executed by the program with a fixed period (e.g., every 0.5 s). Asynchronous tasks are those executed by the program in response to an external event signalled by an interrupt.

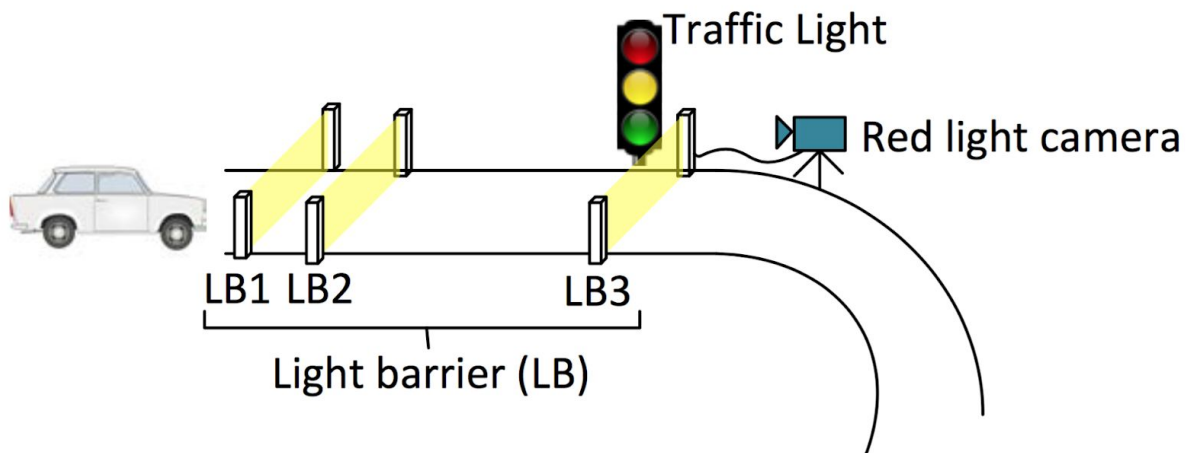


Figure 1: Traffic control system

The system that you will program comprises traffic lights, which control the flow of vehicles on a one-lane entrance to a freeway. The system estimates the speed of vehicles entering the freeway using light barriers LB1 and LB2. A red-light camera monitors the behaviour of drivers; the camera is triggered if light barrier LB3 is breached while the traffic light is red. The system also logs data, counting the number of vehicles that run a red light.

This assignment is to be completed in groups of 2, implemented using the C programming language on an Arduino Uno board. The Arduino Uno board and associated circuitry will be simulated using TinkerCAD Circuits. Your traffic-light controller will be implemented as four subsystems, each of which will be implemented on a

different Arduino Uno board (i.e., each of the four following tasks will be implemented as a new “Circuit” on TinkerCAD).

As with Labs 1 & 2, please read this hand-out carefully before getting started.

Task 1: Basic Traffic Light (Normal Mode)

Implement a basic traffic-light system. The traffic light changes state every second. One cycle is as follows: red to green, green to yellow, yellow to red.

The traffic light will be simulated using three light-emitting diodes (LEDs); one red, one yellow, and one green. Each of these LEDs is connected to a different digital IO pin on an Arduino Uno (e.g., see Figure 2).

Task 2: Configurable Traffic Light (Configuration Mode)

Develop your basic traffic-light system (Task 1) so that it is now configurable. The configurable system can be set to operate in one of four states. In State 1 (the default state), the configurable system is like the basic system, cycling every second. There are three additional states; different states are associated with different cycle periods, as shown in Table 1.

Table 1: Traffic light states

State	Cycle period (s)
1 (default)	1
2	2
3	3
4	4

The traffic lights can only be configured when the system enters “configuration mode”. To enter configuration mode, the user presses a tactile pushbutton (see Figure 2) at any time during a cycle, and in any state of operation (1 through 4). When that button is pressed, the system continues to operate until the next red light, at which point the system enters configuration mode.

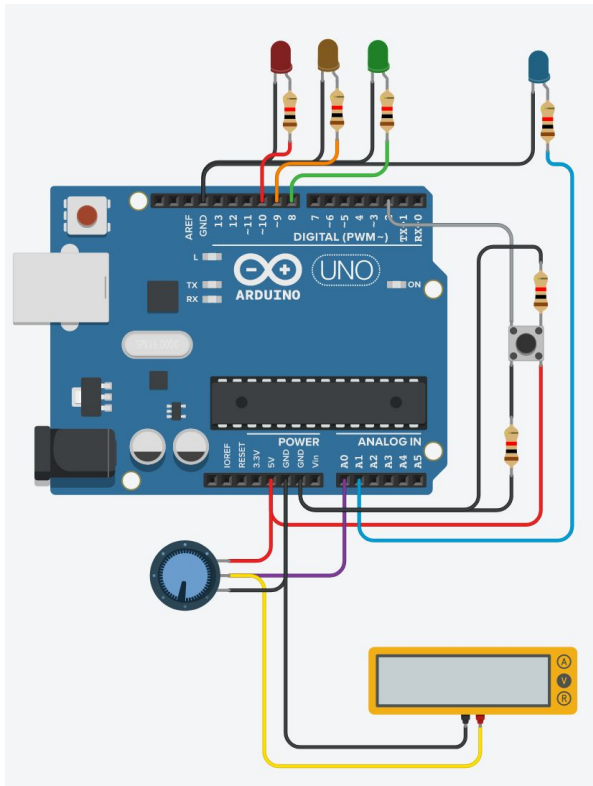


Figure 2: Configurable traffic light control system

In configuration mode:

- The traffic light should stay red.
- A fourth LED (LED4; see blue LED at top-right of Figure 2) should be used to represent the current state of the traffic lights: LED4 encodes a state number, x , by blinking x times in 1 second, and then remaining off for 2 seconds. For example, in State 3, LED4 should issue 3 pulses (each pulse period = 0.33 s; duty cycle = 50%) and then remain off for 2 seconds. In State 4, LED4 should issue 4 pulses (pulse period = 0.25 s; duty cycle = 50%) and then remain off for 2 seconds. This three-second cycle should repeat for as long as the system remains in configuration mode.
- States are selected using a potentiometer via ADC input (see Figure 2). The full range of ADC outputs should be used when selecting a State. For example, if an

8-bit ADC produces 256 digital words/codes, then words/codes 0 through 63 should be used to select State 1, 64 through 127 to select State 2, and so on.

To exit configuration mode, the user presses the tactile push button again; traffic light operation then resumes in the newly selected state. When the system is not in configuration mode, LED4 should be constantly illuminated.

Task 3: Speed Monitor

Implement a system that estimates the speed of vehicles as they approach the freeway. The speed of vehicles is estimated using the light barriers LB1 and LB2. To estimate the speed of a vehicle, the system first computes the difference between (1) the time LB1 is breached, and (2) the time LB2 is breached (the “elapsed time”). Then, assuming LB1 and LB2 are separated by 20 metres, it computes an estimate of speed. It is safe to assume that only one vehicle at a time will pass between LB1 and LB2. This means LB1 will always be triggered first, followed by LB2.

The light barriers LB1 and LB2 are simulated using tactile push buttons, as illustrated in Figure 3; by pressing the left button we simulate the breach of LB1, and by pressing the right button we simulate the breach of LB2. The speed estimate, in units of km/h, is to be represented using a pulse-width modulated (PWM) signal (pulse period = 1 s). You should write this PWM signal to one of the Arduino Uno digital IO pins, and represent the signal using an oscilloscope (Figure 3). The encoding of speed is as follows: PWM signal duty cycle is directly proportional to estimated speed. For example, if the estimated speed is 10 km/h, the PWM signal duty cycle = 10%. For 20 km/h, then duty cycle = 20%, and so on. If the speed estimate ≥ 100 km/h, then duty cycle = 100%. The PWM signal should persist until another vehicle passes between LB1 and LB2.

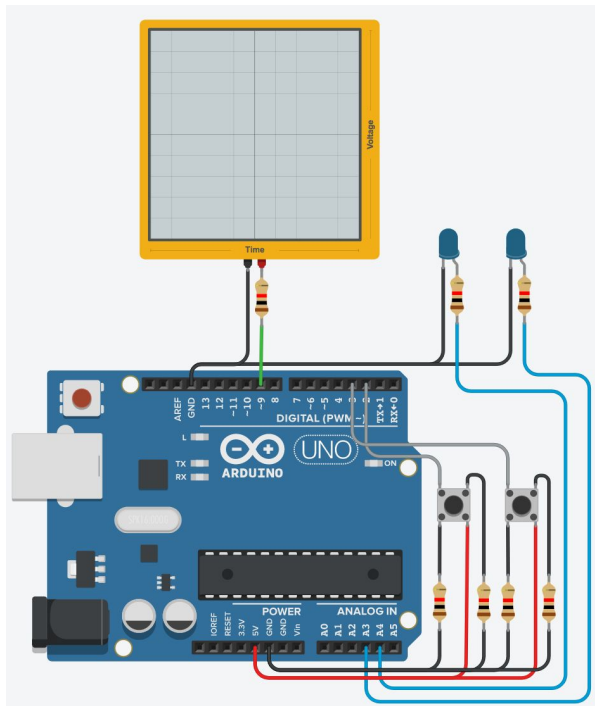


Figure 3: Circuit simulating the speed monitor system

The plot below (Figure 4) illustrates speed versus elapsed time for an ideal speed monitor system. If a vehicle is travelling very fast (e.g., 150 km/h), then small errors in the estimate of elapsed time will cause a relatively large error in the speed estimate. The errors associated with the speed estimates of the system you implement should be no greater than 1 km/h for speeds up to 150 km/h. (A speed of 150 km/h corresponds to an elapsed time of 0.480 s, and 151 km/h corresponds to an elapsed time of 0.477 s. This 3 ms difference means the response time of your system to breach of LB1 or LB2 must be less than 1.5 ms.)

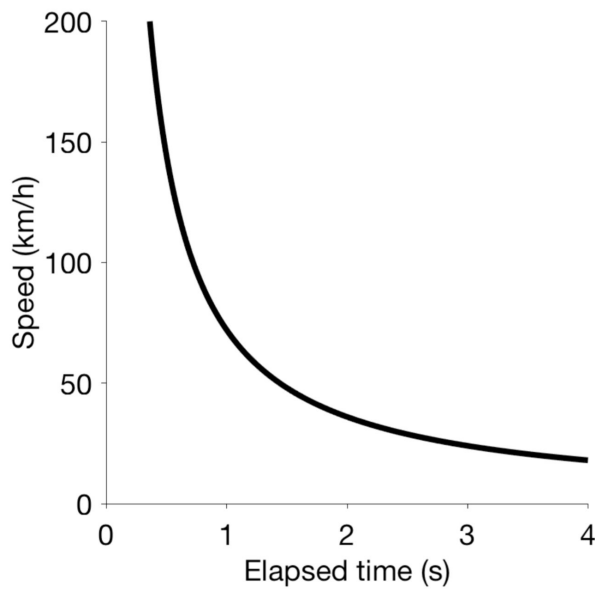


Figure 4: Speed-versus-elapsed time for an ideal speed monitor system. Elapsed time = time of LB2 breach - time of LB1 breach. Because LB1 and LB2 are separated by 20 m, then an elapsed time of 0.72 s, for example, corresponds to a speed of 100 km/h.

Task 4: Red-Light Camera

Implement a red-light camera. The traffic light cycles as normal (i.e., State 1). The camera is triggered if the traffic light is red, and a vehicle breaches light barrier LB3. You may find it useful to re-use your code from Task 1 to simulate the cycling of the traffic light.

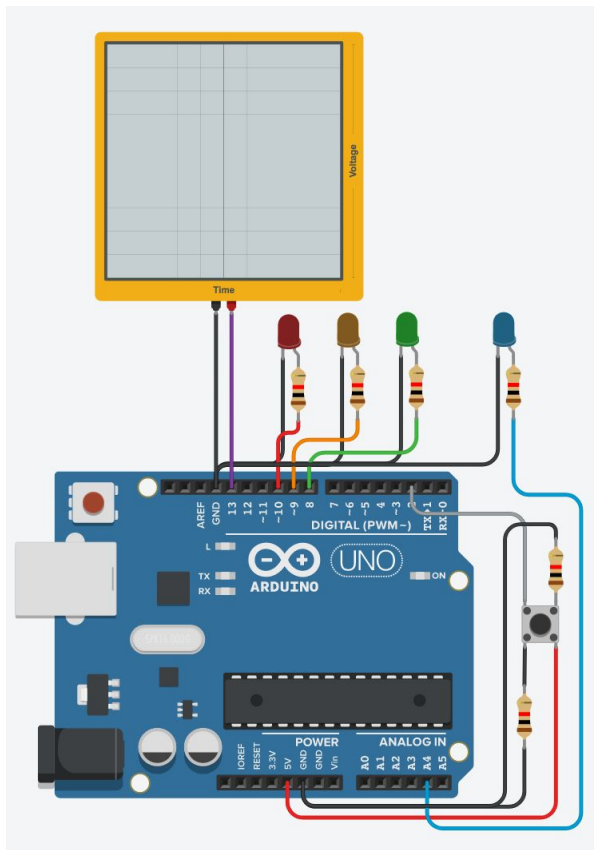


Figure 5: Circuit simulating a red-light camera

The light barrier LB3 is simulated using a tactile pushbutton, as illustrated in Figure 5. By pressing the button we simulate the breach of LB3. To show that the camera has been triggered, an additional LED (LED_C; blue LED shown at right in Figure 5) should be pulsed twice (pulse period = 0.5 s; duty cycle = 50%). The flashing of LED_C should not otherwise affect the running of your system. When light barrier LB3 is breached, the system must respond within 10 ms (enabling an image of the vehicle's number plate to be taken before the vehicle leaves the camera's frame).

The system should keep track of the total number of cars that have triggered the red-light camera. This count is to be encoded using a pulse-width modulated (PWM) signal (pulse period = 1 s). You should write this PWM signal to an Arduino Uno digital IO pin, and represent the signal using an oscilloscope (Figure 5). The encoding of this count is as follows: PWM signal duty cycle is directly proportional to the count. For example, if the count is 10, the PWM signal duty cycle = 10%. For 20, then duty cycle = 20%, and so on. If the count ≥ 100 , then duty cycle = 100%. The PWM signal should persist until the count increases.

Marking Criteria

This assignment is worth 20% of your final grade for MECHENG 313.

Software (10%). Your code will be assessed based on its readability (good commenting and clear, consistent style) and your technical proficiency. You are expected to use low-level C, as described in lectures, and avoid using the Arduino application programming interface (API) as much as possible. TAs will use the code you submit on Canvas to simulate the circuits you have built on TinkerCAD Circuits. During simulations, TAs will check that your systems have been implemented according to the above-described specifications.

Report (10%). Write a report describing your system (12pt font, single-spaced). Your report should comprise the following sections: Introduction, Methods, Results, Discussion. Your Introduction should run to approximately half a page. There, you should give an overview of your system; this overview should be pitched to a non-specialist mostly unfamiliar with microcontrollers and embedded systems (e.g., a Part 3 student enrolled in Civil Engineering). In Methods, you should describe your system in sufficient detail such that a specialist familiar with the Arduino Uno and the ATmega328P can reproduce your implementation (e.g., pitch your Methods section to a fellow Part 3 Mechatronics student). In Results, describe how your design enabled the system to meet the following two deadlines:

1. Red-light camera: “When light barrier LB3 is breached, the system must respond within 10 ms.”
2. Speed monitor: “The errors associated with the speed estimates of the system you implement should be no greater than 1 km/h for speeds up to 150 km/h.”

In Discussion, you should describe any nontrivial and/or interesting design decisions that you made, making reference to real-time concepts described in lectures (e.g., was programmed IO an appropriate solution to a design problem, or is all IO interrupt-driven?) Your Discussion should run to no more than 1 page. Overall, your report should be no more than 5 pages, including any necessary plots, images, and/or appendices.



Files to Submit

Files are to be submitted on Canvas.

Software submission. One submission per group. Please submit a zip file. This zip file should contain several C source code files (“example_filename.c”), as well as a “README.txt” text file. The README.txt file should list names and UPIs of group members. It should also describe clearly which C source code file goes with which of your TinkerCAD Circuits.

Report. One submission per group. Please submit a PDF.

Peer Review. One submission per person. Please use the form provided.

